

# Electricity

## Knowledge

### Electricity

associate the brightness of a lamp or the volume of a buzzer with the number and voltage of cells used in the circuit

compare and give reasons for variations in how components function, including the brightness of bulbs, the loudness of buzzers and the on/off position of switches



use recognised symbols when representing a simple circuit in a diagram

## Working Scientifically

Systematically identifying the effect of changing one component at a time in a circuit

Designing and making a useful circuit.

## Hook into a Book

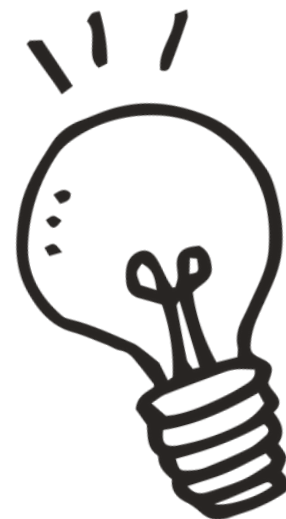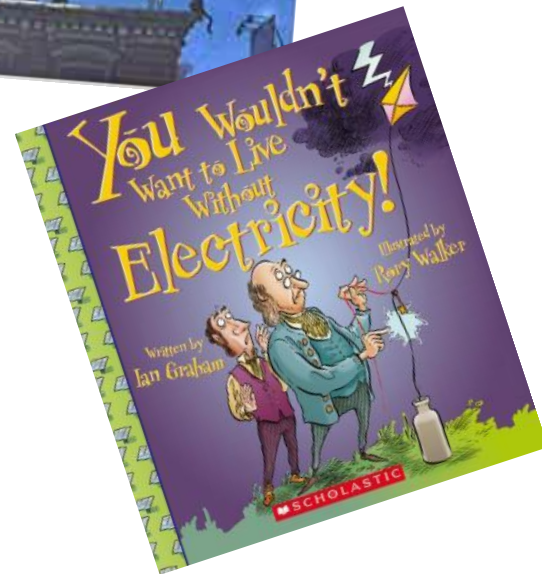

## Activate Prior Knowledge

### KS2

- I can identify common appliances that run on electricity
- I can construct a simple series electrical circuit, identifying and naming its basic parts, including cells, wires, bulbs, switches and buzzers
- I can identify whether or not a lamp will light in a simple series circuit, based on whether or not the lamp is part of a complete loop with a battery
- I can recognise that a switch opens and closes a circuit and associate this with whether or not a lamp lights in a simple series circuit
- I can recognise some common conductors and insulators, and associate metals with being good conductors.

## Key Vocabulary

<b>circuit</b>	A path that an electrical <b>current</b> can flow around.
<b>symbol</b>	A visual picture that stands for something else.
<b>cell/battery</b>	A device that stores chemical energy until it is needed. A <b>cell</b> is a single unit. A <b>battery</b> is a collection of <b>cells</b> .
<b>current</b>	The flow of <b>electrons</b> , measured in <b>amps</b> .
<b>amps</b>	How electric <b>current</b> is measured.
<b>voltage</b>	The force that makes the electric <b>current</b> move through the wires. The greater the <b>voltage</b> , the more <b>current</b> will flow.
<b>resistance</b>	The difficulty that the electric <b>current</b> has when flowing around a <b>circuit</b> .
<b>electrons</b>	Very small particles that travel around an electrical <b>circuit</b> .

Investing in



the UNIQUENESS

of each individual

"I Am Fearfully And Wonderfully Made"  
– Psalms 139 v14



## Key Knowledge
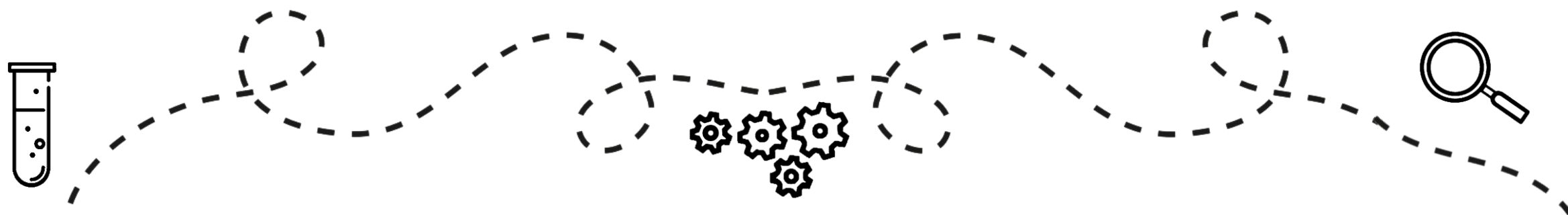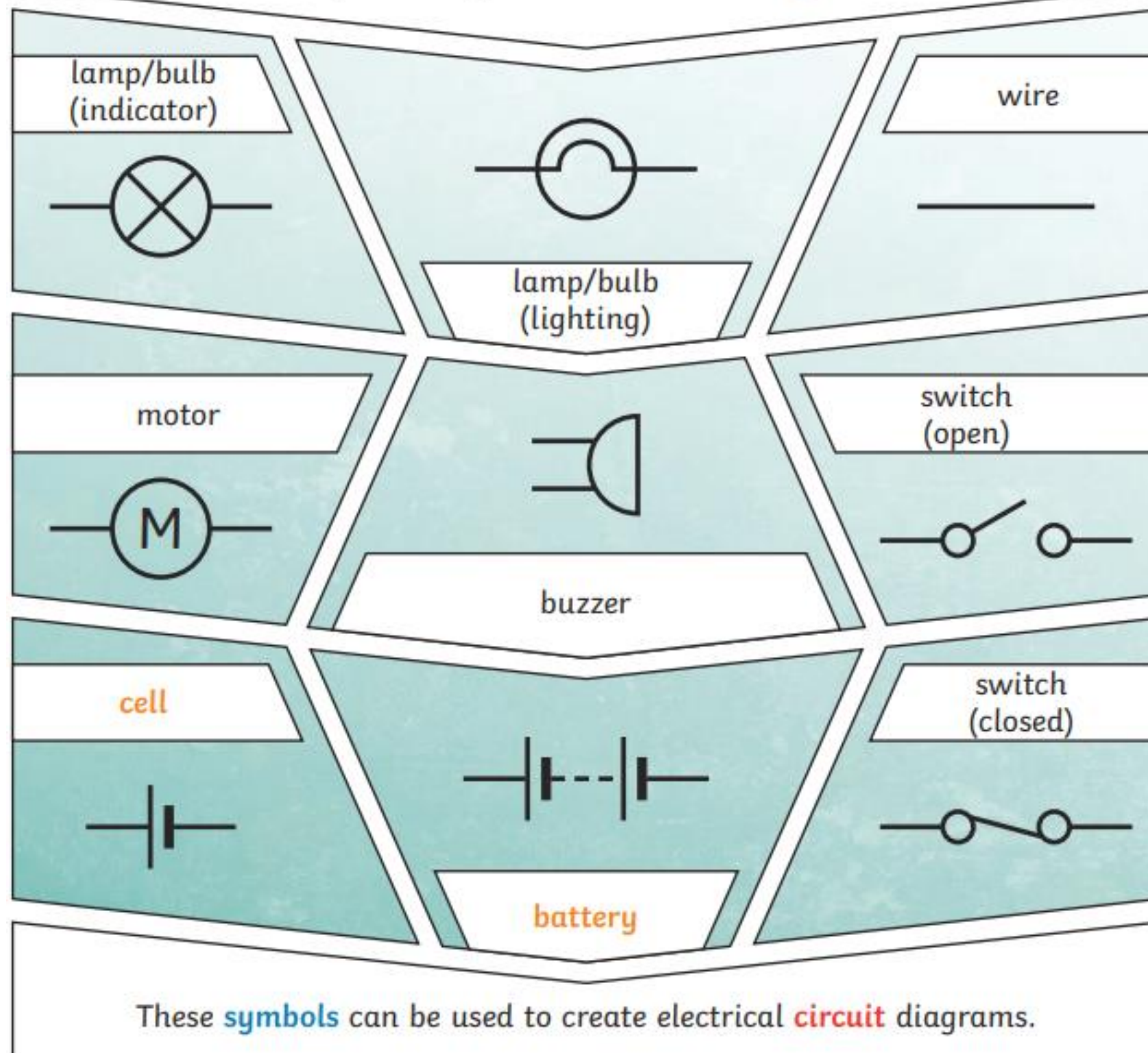
### Components of a **Circuit** and Their **Symbols**



What will make a bulb brighter or a buzzer louder?

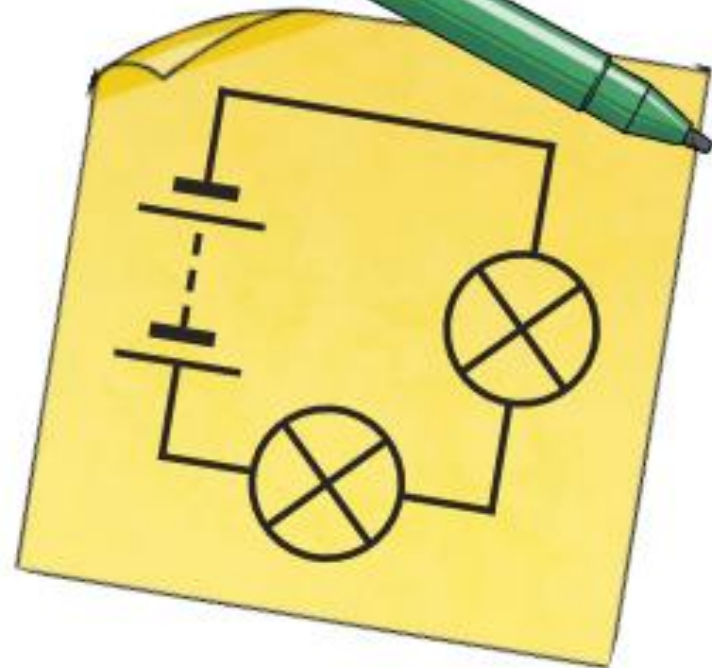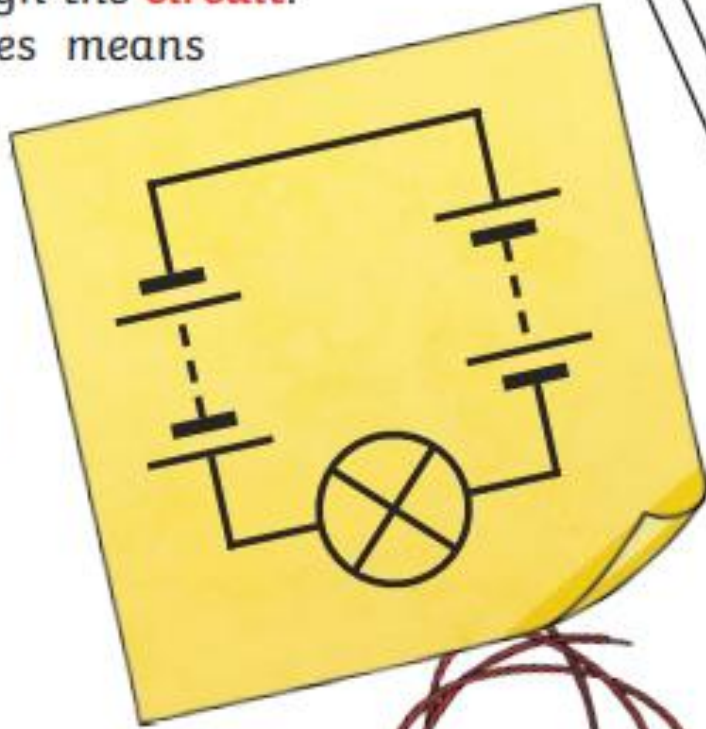- More **batteries** or a higher **voltage** create more power to flow through the **circuit**.
- Shortening the wires means the **electrons** have less **resistance** to flow through.



### Series Circuit

A **circuit** that has only one route for the **current** to take. If more bulbs or buzzers are added, the power has to be shared and so they will be dimmer or quieter. If just one part of this series **circuit** breaks, the **circuit** is broken and the flow of **current** stops.

What will make a bulb dimmer or a buzzer quieter?

- Fewer **batteries** or a lower **voltage** give less power to the **circuit**.
- More buzzers or bulbs mean the power is shared by more components.
- Lengthening the wires means the **electrons** have to travel through more **resistance**.

